
 



_XOR

 


... is equivalent to ...




mux4_1

 

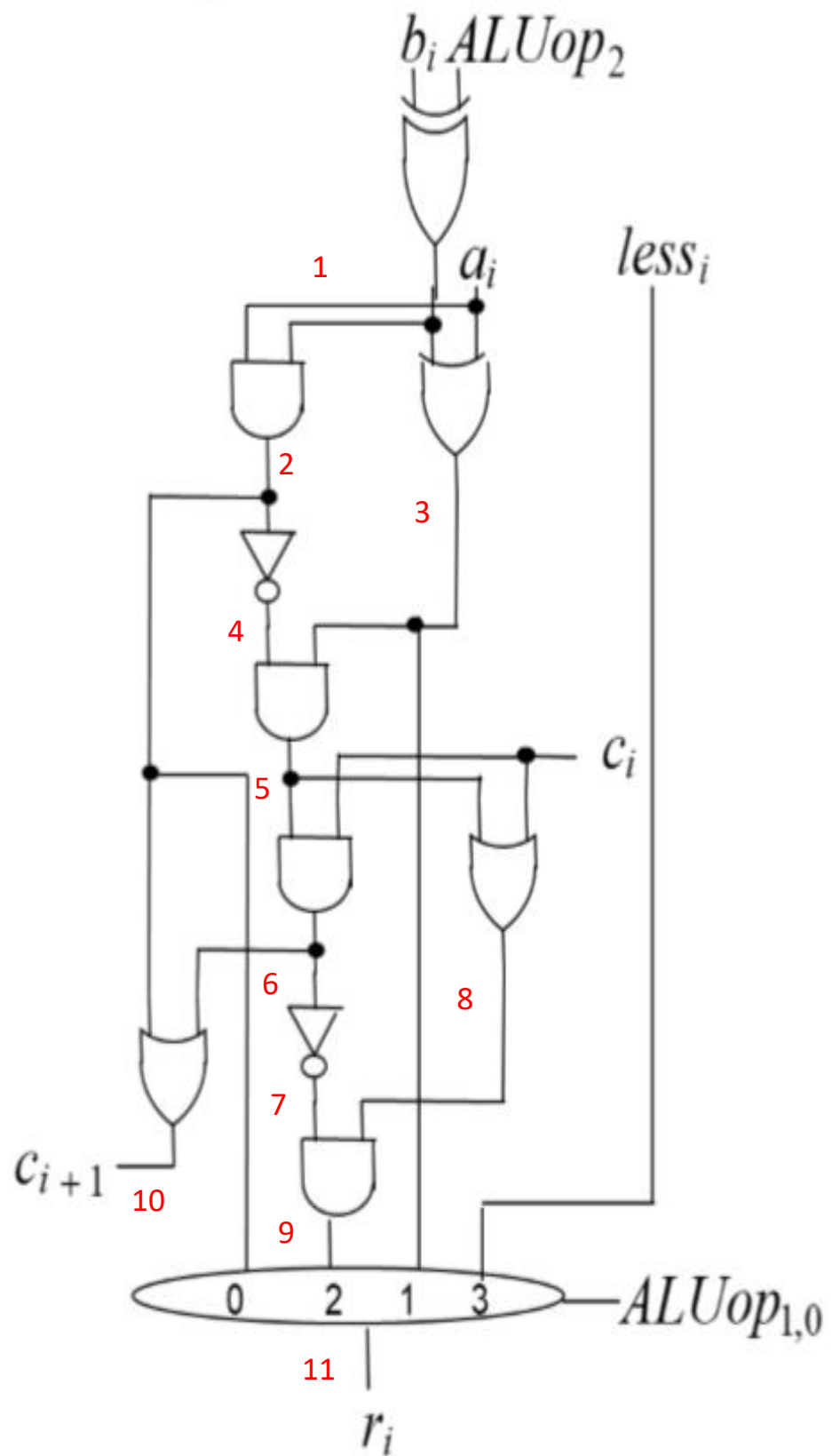1-bit ALU module will be designed same as shown below:




ALU32bit

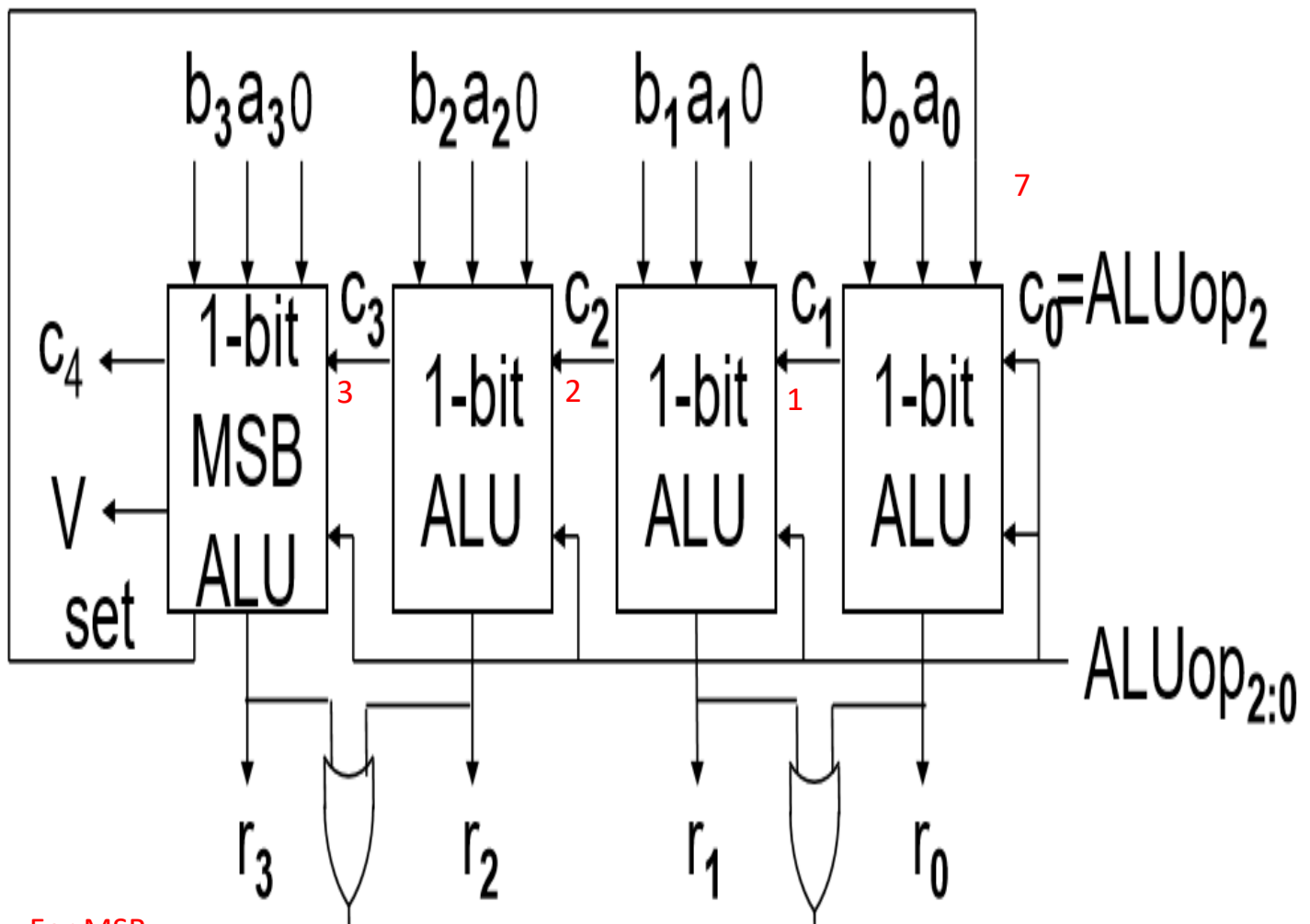

For MSB

for MSB

the MSB
to indicate
the result.

 

Each number represent a comment in verilog code, you can see which number operation happens which line .

For example :

```
module _xor( result, input1, input2);  
input input1, input2 ;  
output result ;  
wire notInput1 , notInput2, result_input1, result_input2 ;  
  
not not_input1( notInput1, input1 ) ; // 1  
not not_input2( notInput2, input2 ) ; // 2  
  
and before_result1( result_input1, notInput1, input2 ) ; // 4  
and before_result2( result_input2, notInput2, input1 ) ; // 3  
  
or now_result( result, result_input1, result_input2); // 5  
endmodule
```

```
module mux4_1( result, S1, S0, I0, I1, I2, I3);  
  
input I0, I1, I2, I3;  
input S0, S1 ;  
  
output result ;  
  
wire not_S1, not_S0 ;  
wire and_input0, and_input1, and_input2, and_input3 ;  
  
not notS1( not_S1, S1 ) ; // 2  
not notS0( not_S0, S0 ) ; // 1  
  
and andInput0( and_input0, not_S1, not_S0, I3 ) ; // 3  
and andInput1( and_input1, not_S1, S0, I2 ) ; // 4  
and andInput2( and_input2, S1, not_S0, I1 ) ; // 5  
and andInput3( and_input3, S1, S0, I0 ) ; // 6  
  
or create_result( result, and_input0, and_input1, and_input2, and_input3 ); // 7  
endmodule
```